

Designing Power For Sensitive Circuits

Steve Sandler, Picotest

steve@picotest.com


+1-480-375-0075

What are sensitive circuits?

Many low power circuits are **hyper-sensitive** to power supply noise.

Examples of hyper-sensitive circuits include clock oscillators (XOs), low noise amplifiers (LNAs), phase locked loops (PLLs), mixers and precision voltage references to name just a few.

Sensitivity to power supply noise



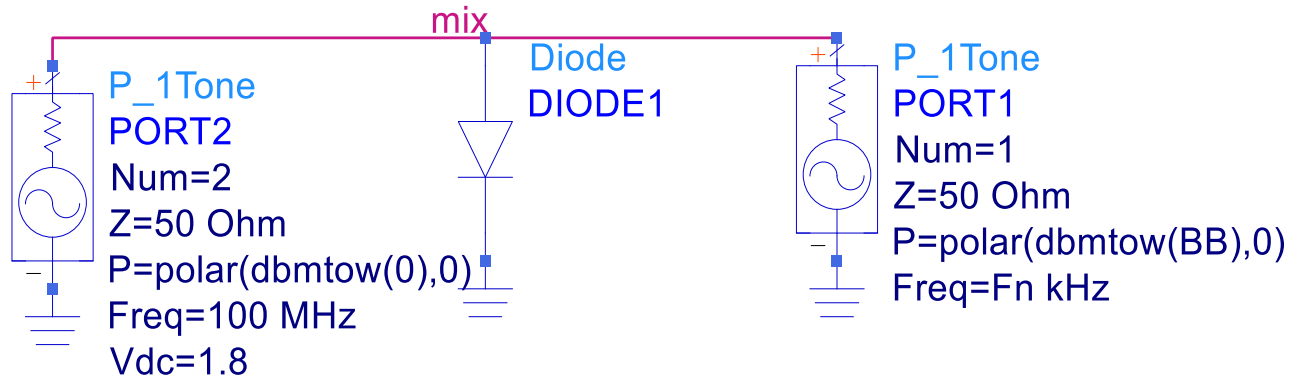


HARMONIC BALANCE


HarmonicBalance
 HB1
 Freq[1]=100 MHz
 Freq[2]=Fn kHz
 Order[1]=1
 Order[2]=15




VAR
 VAR1
 Fn=500
 BB=-65 {t}

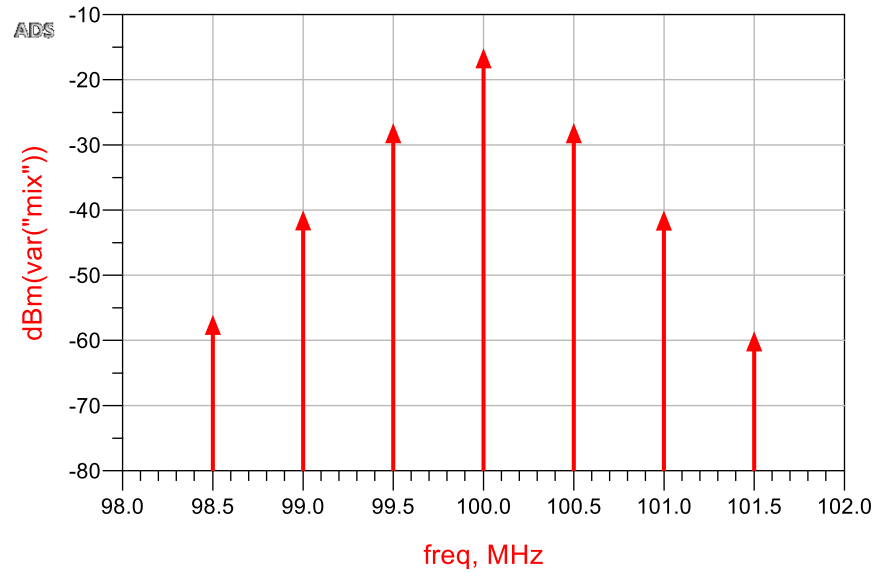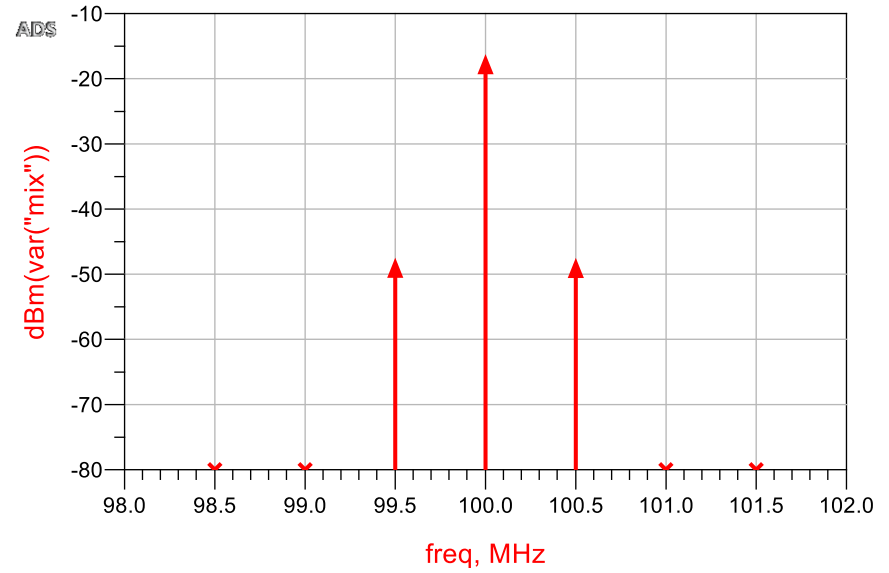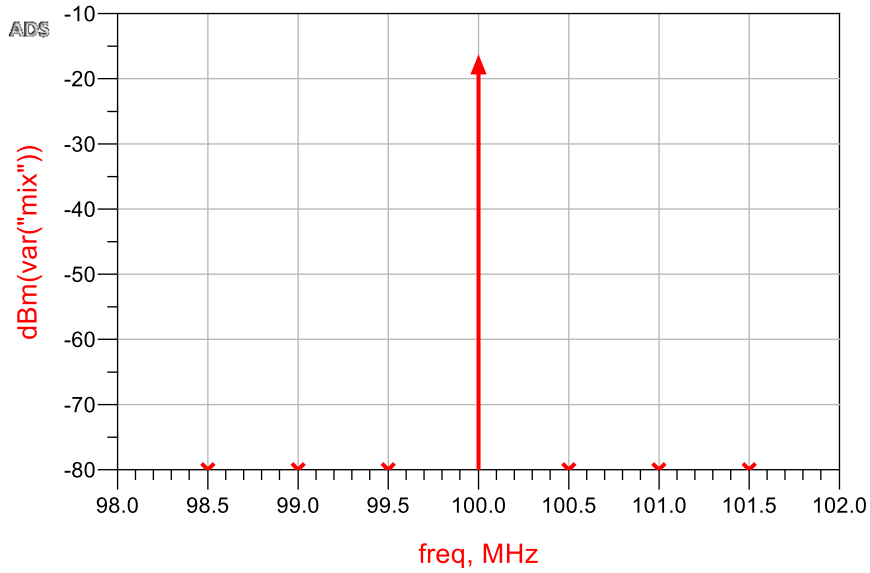


Defining Sensitivity

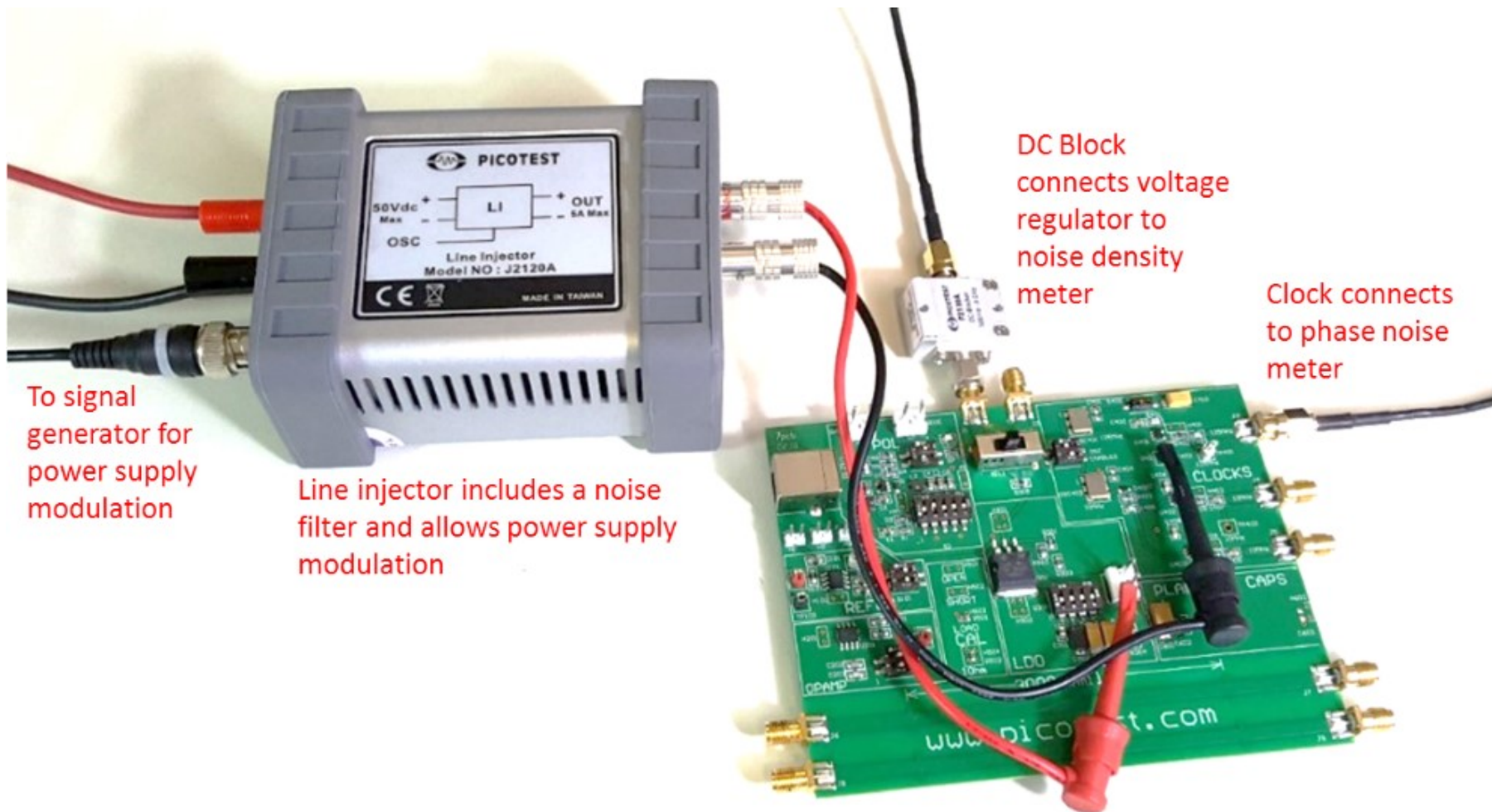

Not all sensitive circuits are sensitive

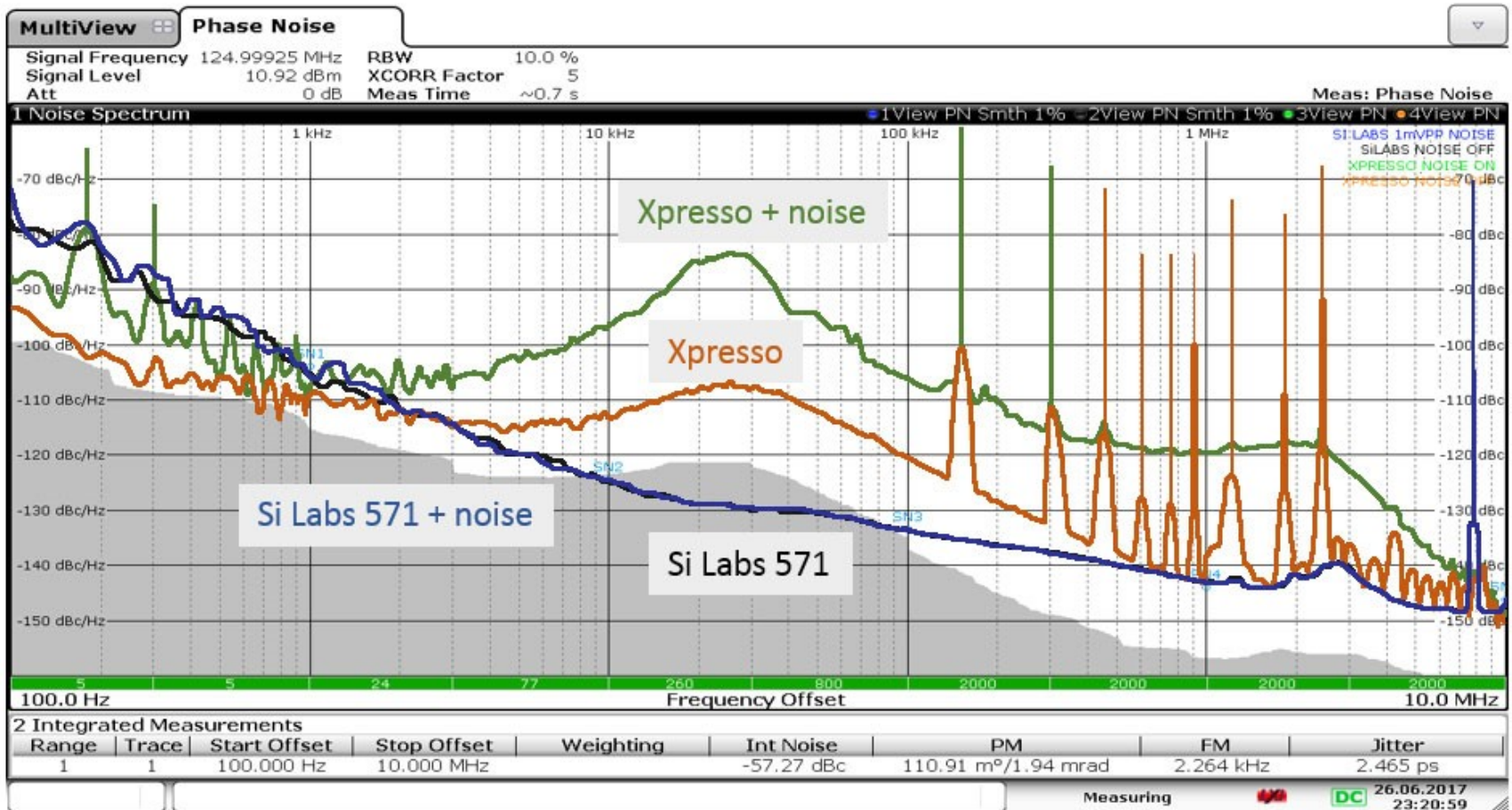


Noise Density 3 Voltage Regulators

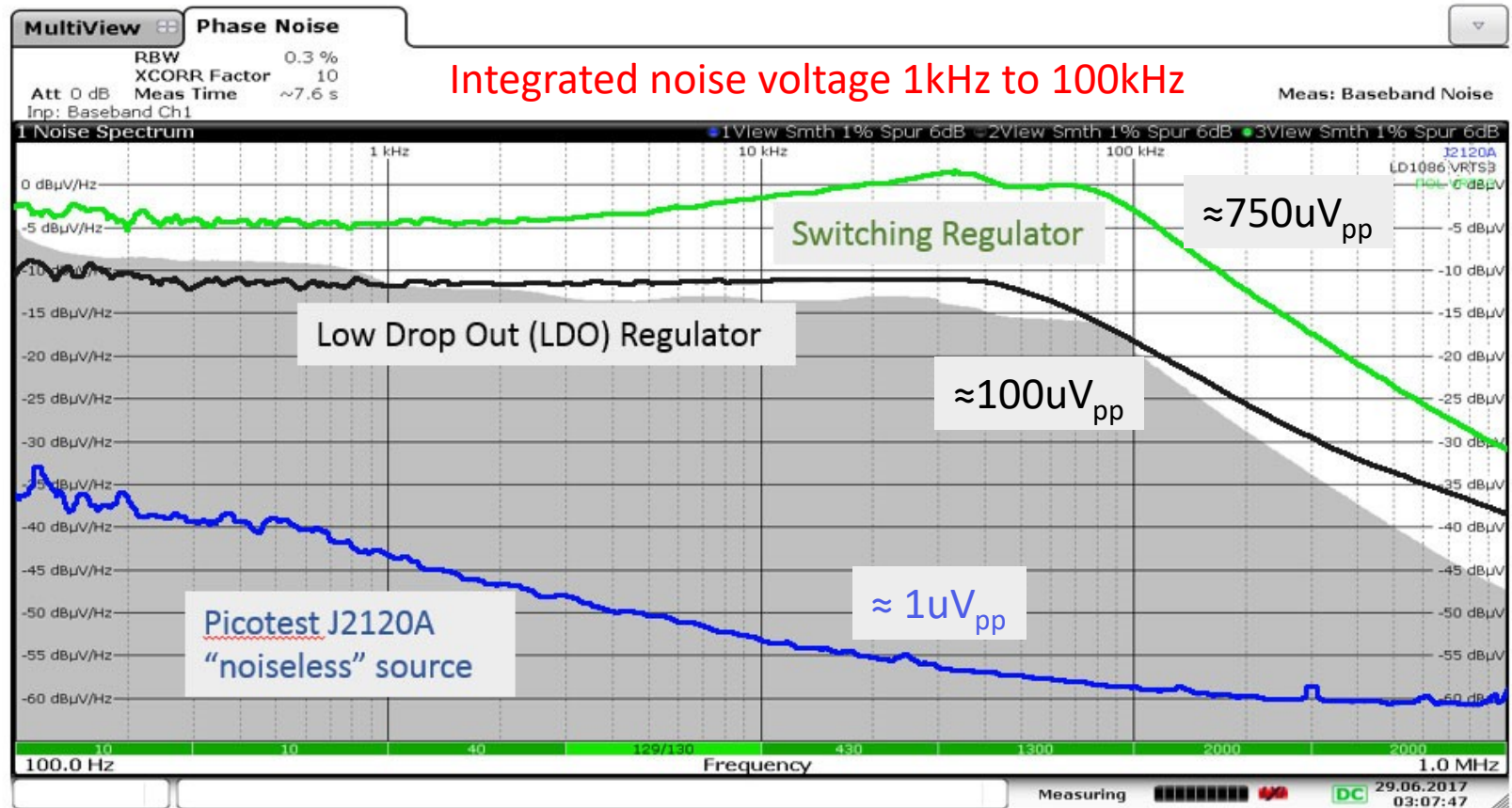


Switching Regulator Noise Density

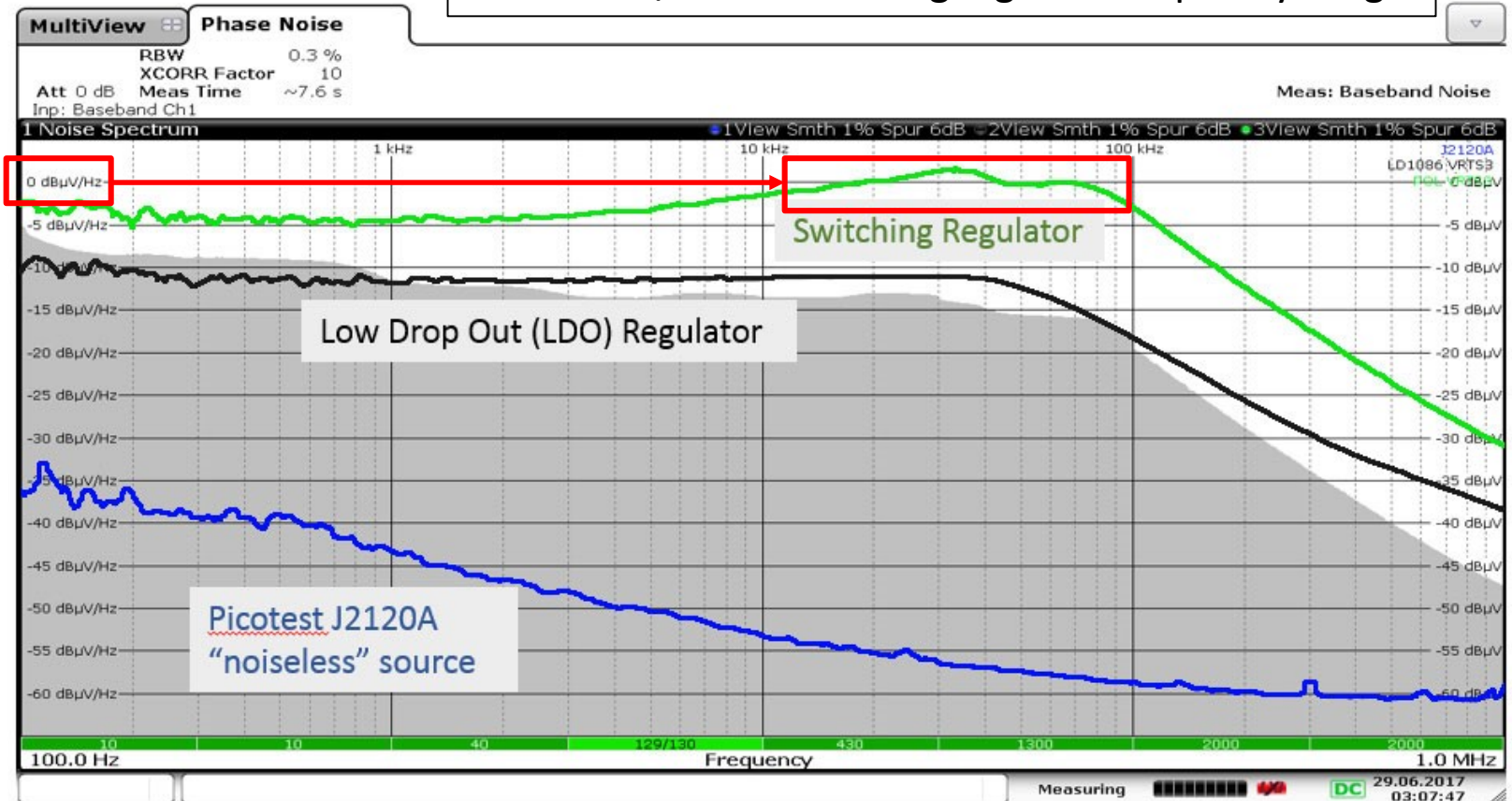
The switching regulator noise density is a little above $1\mu\text{V}/\sqrt{\text{Hz}}$ in the highlighted frequency range



Phase Noise 3 Voltage Regulators

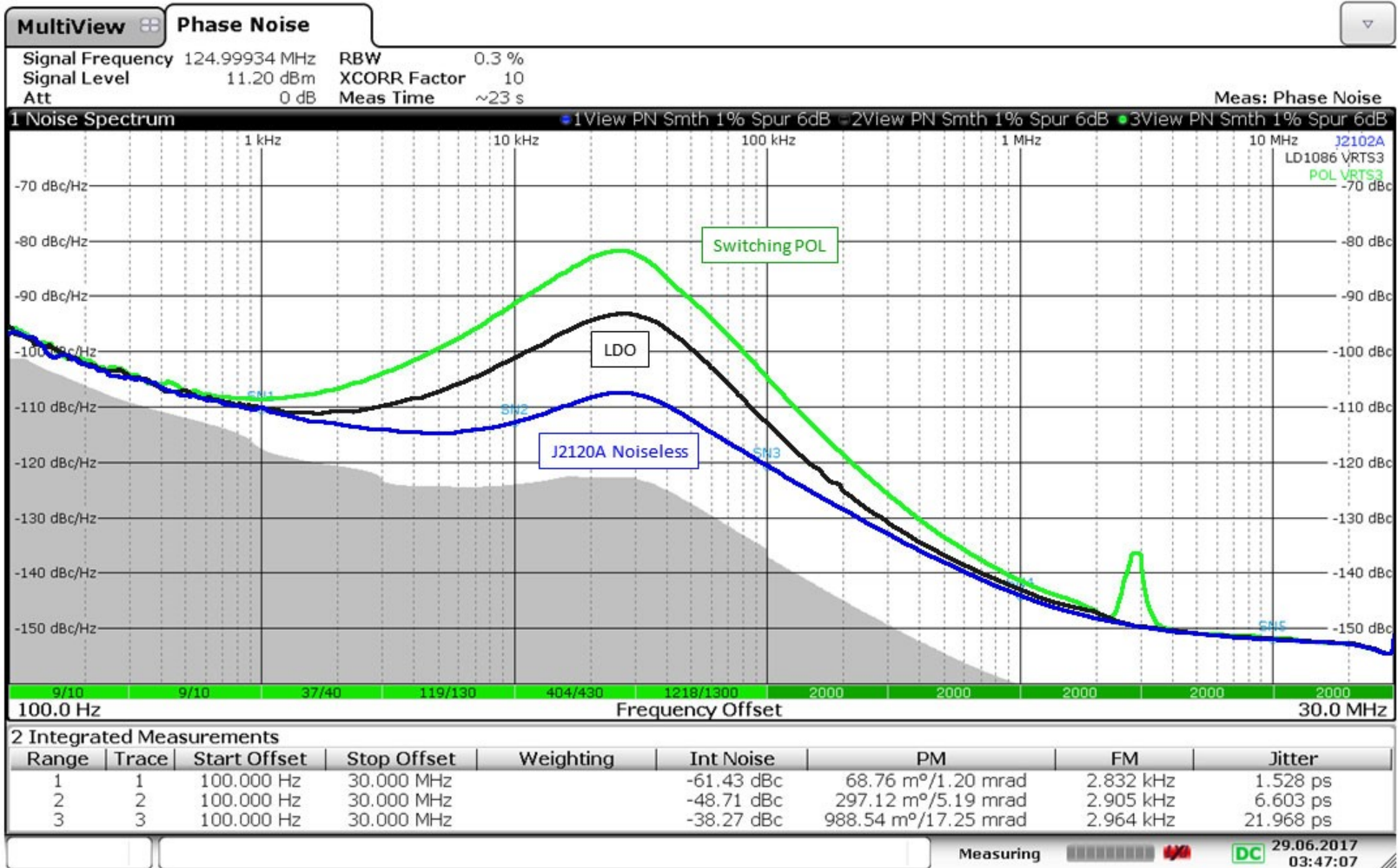

Assessing the Damage

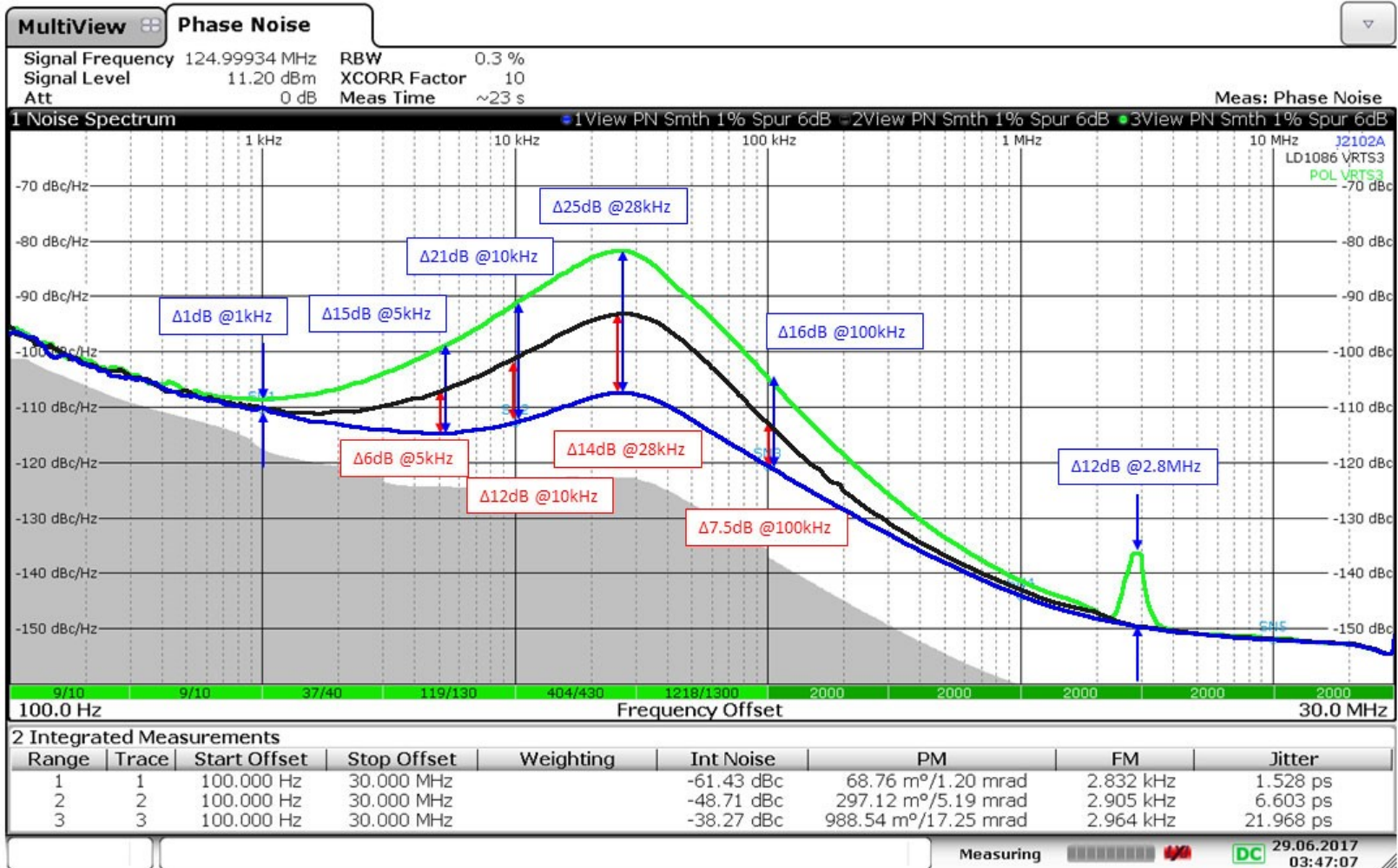

Simplest Noise Filter


Regulation and noise are not the same thing and counterintuitively they oppose each other

How much voltage can you give up?


$$R1 = \frac{100mV}{I_{dc}} = \frac{100mV}{39mA} = 2.60\Omega$$

$$C1(dB, f) = \frac{0.159 \cdot \sqrt{e^{0.2303 \cdot dB}} \cdot e^{-0.115 \cdot dB} \cdot \sqrt{e^{0.2303 \cdot dB} - 1}}{R \cdot f}$$

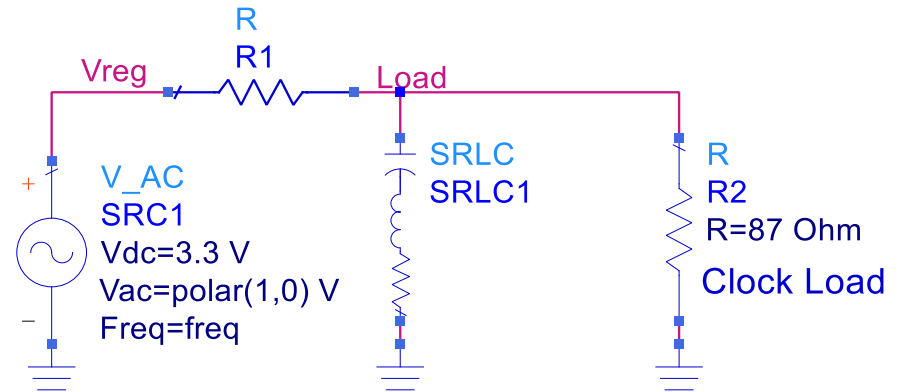
$$ESR_{max} = \frac{0.707 \cdot R}{e^{0.115 \cdot dB_{max}} - 1}$$



Determining the Capacitor

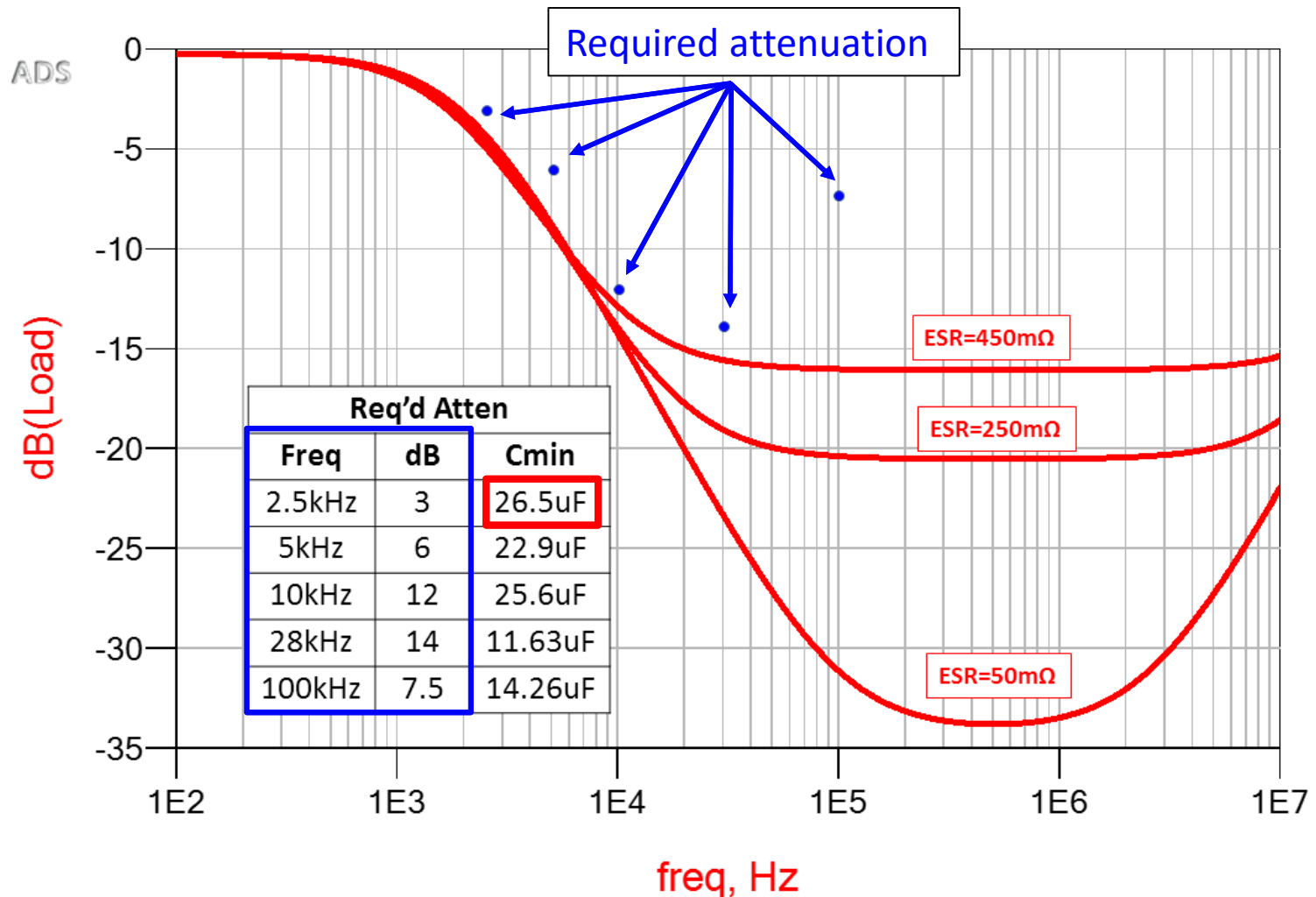


33uF/30mΩ ESR + 2.4Ω Filter

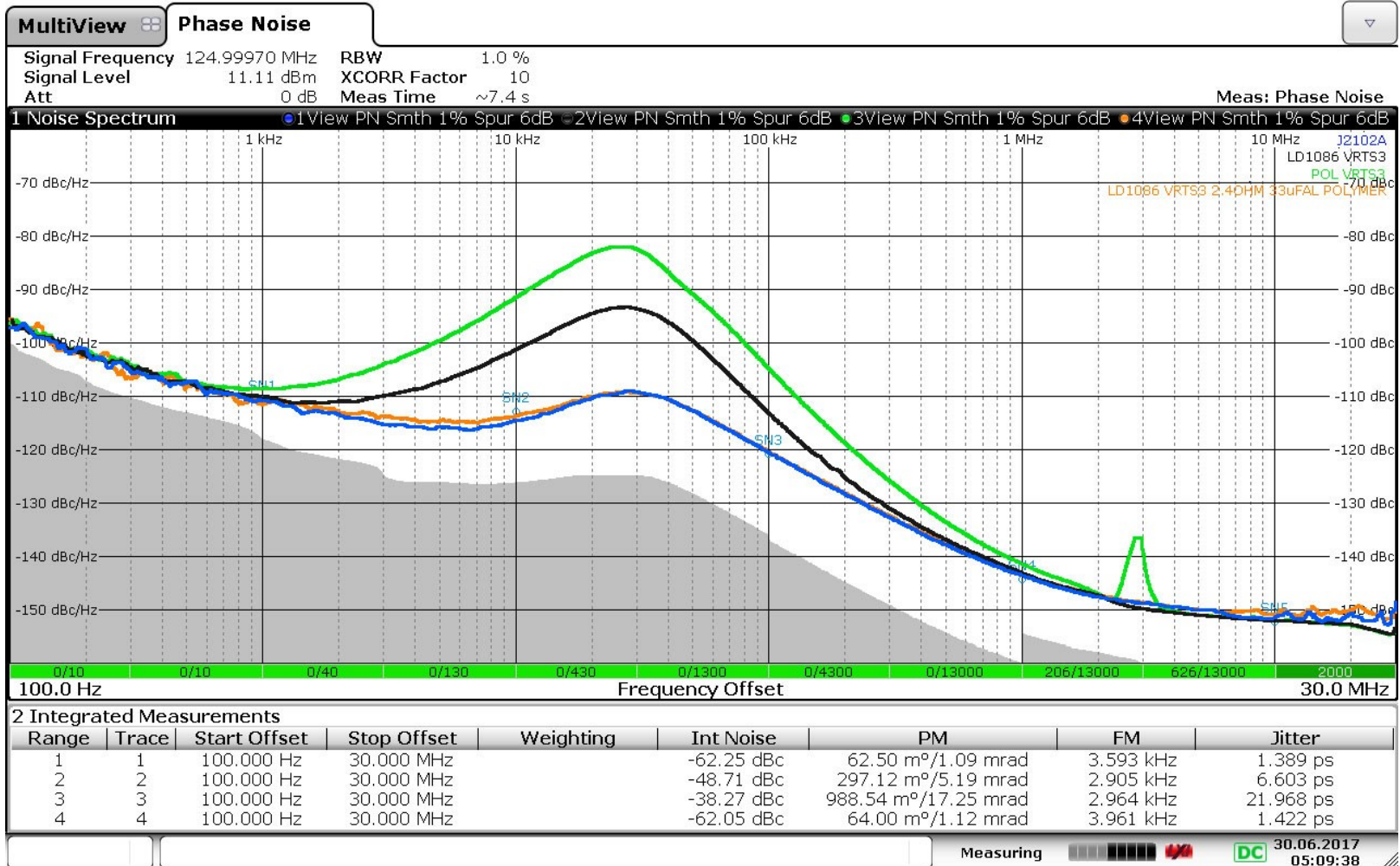


Unexpected Noise – 2.8MHz POL


2017-06-26 04:45:11

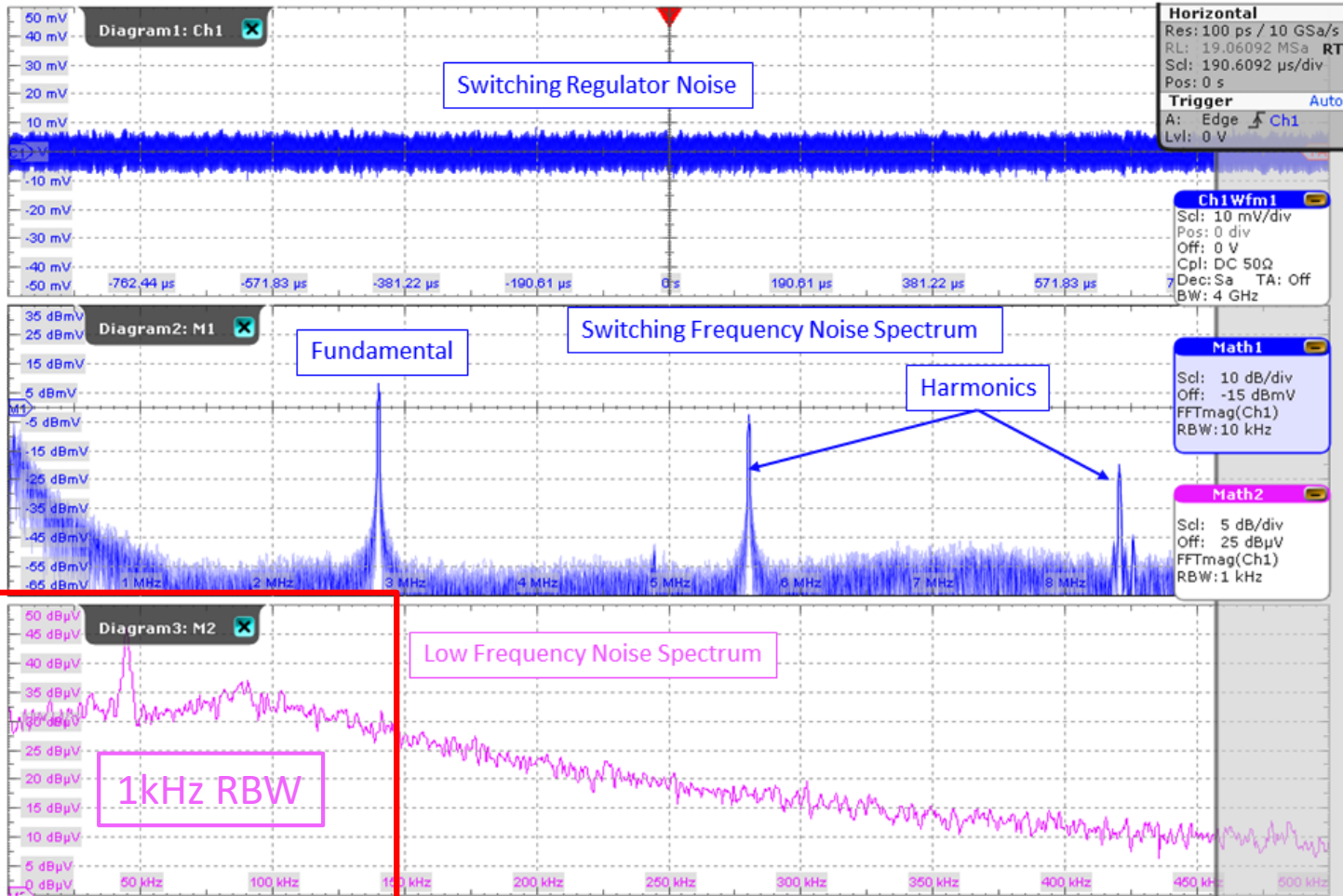

Why The Low Frequency Noise?

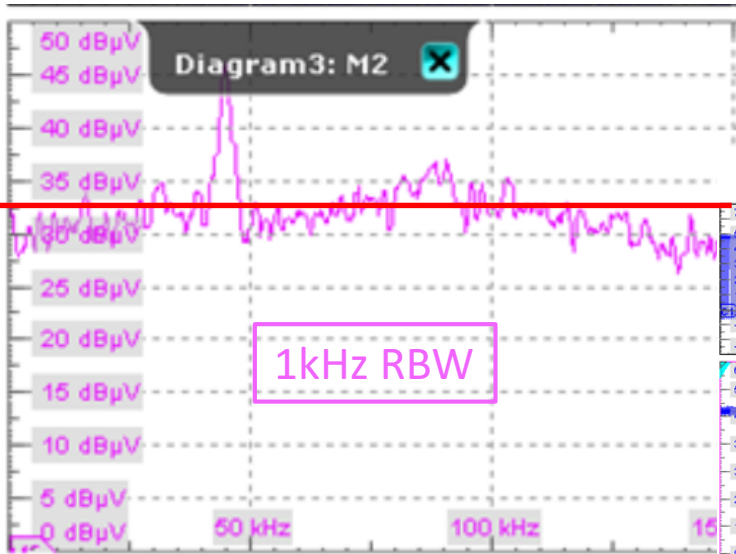

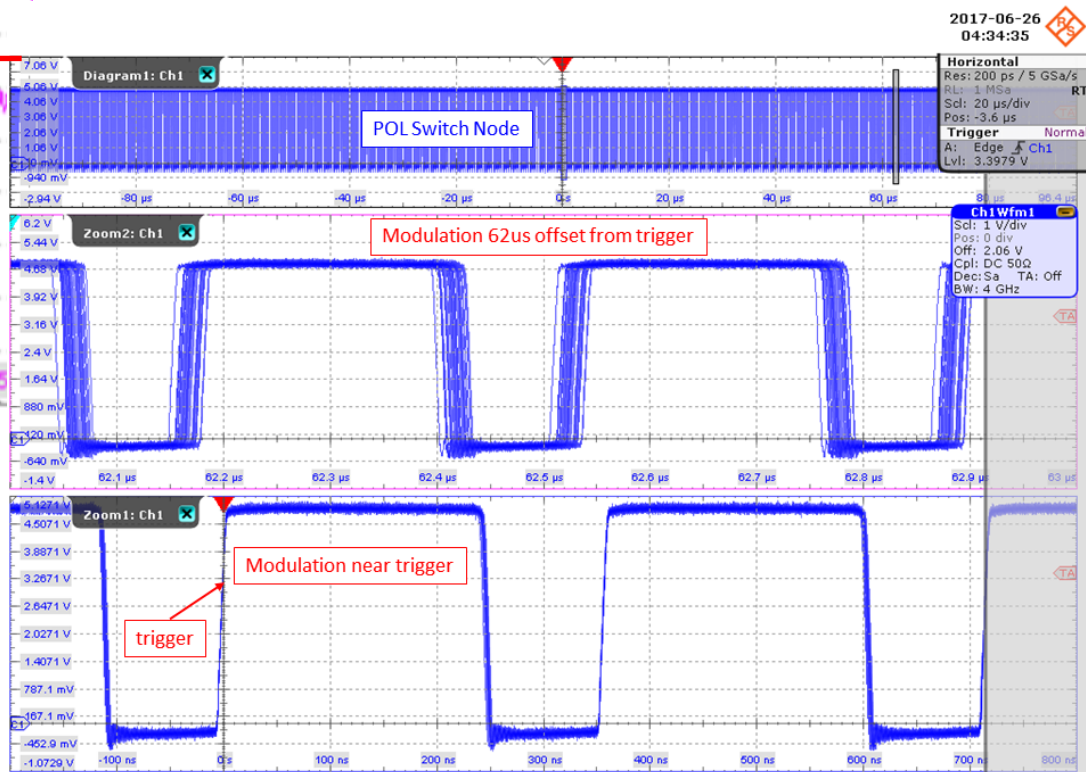This is in very good agreement with the signal source analyzer noise density measurement




32dBuV at 1kHz RBW (40uVpk)

$$32dBuV \cdot \sqrt{\frac{1Hz}{1kHz(RBW)}} \cong 1.2uV/\sqrt{Hz}$$

The modulation noise is accounted for

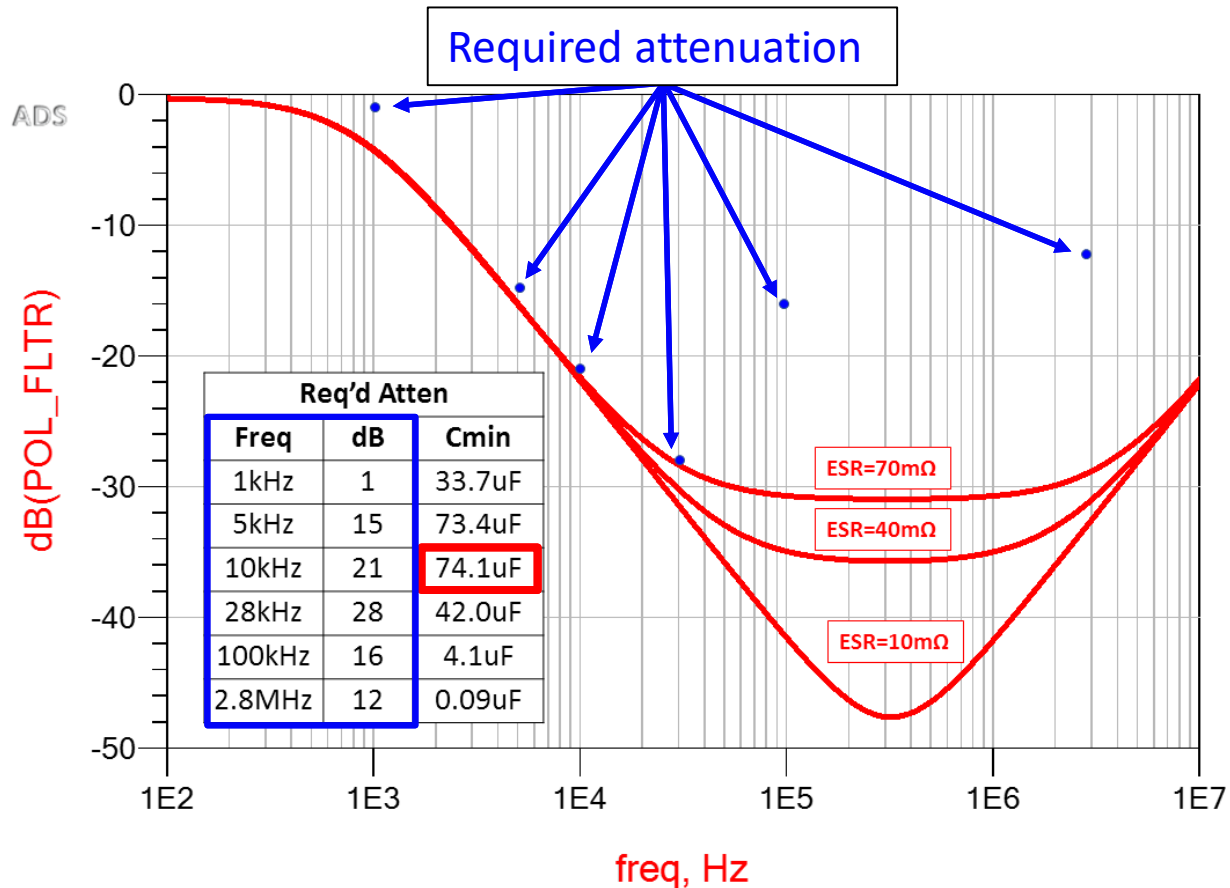Despite the 2.8MHz switching frequency it's the 10kHz range that defines the filter



About Ferrite Beads

For Q=0.5


$$L_{max} = 0.5 \cdot C \cdot R^2$$

IF R approaches zero

then **NO INDUCTANCE ALLOWED**


$$ESR_{max} = \frac{0.707 \cdot R}{e^{0.115 \cdot dB_{max}} - 1}$$
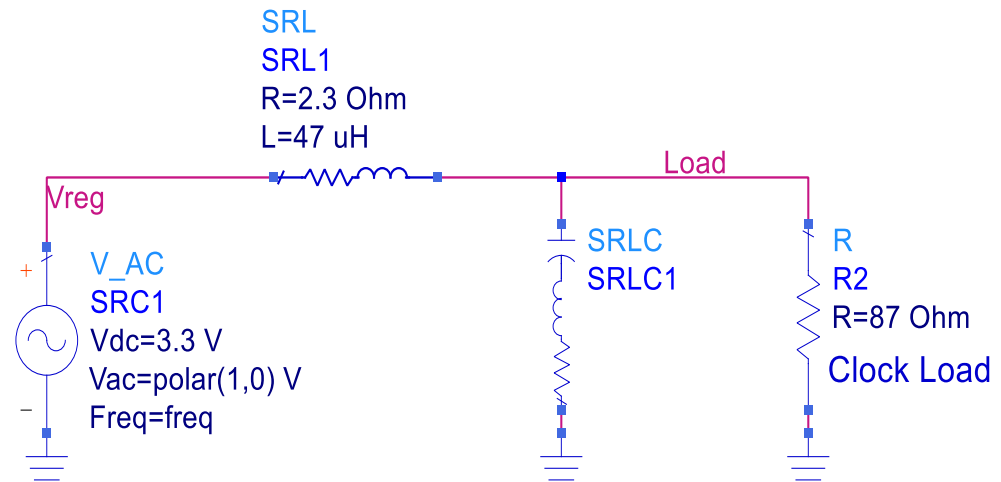
$$R = \frac{100mV}{I_{dc}} = \frac{100mV}{39mA} = 2.60\Omega$$






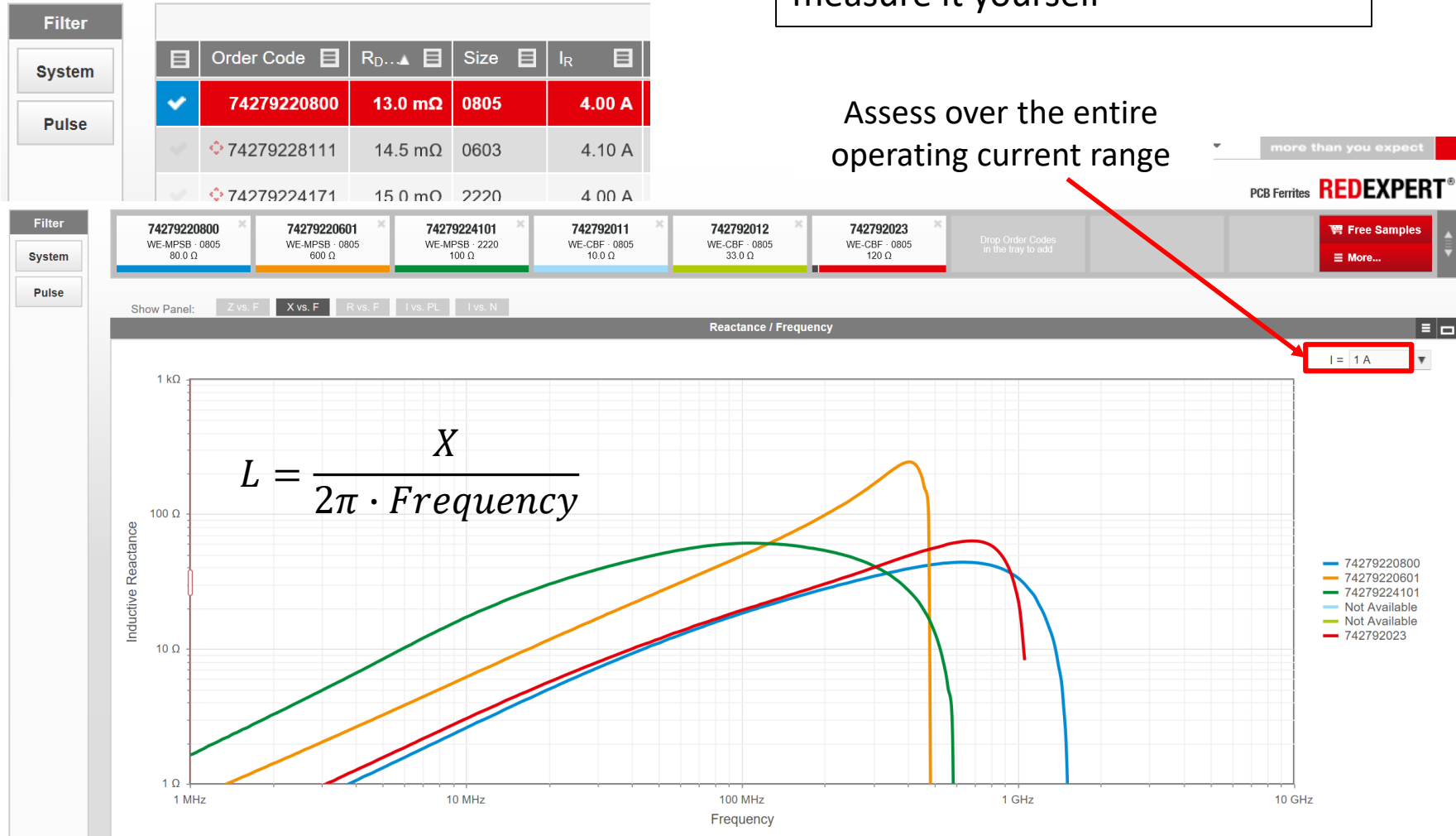Bead datasheets generally include DCR and high frequency resistance, but look for Inductive reactance and DC Bias data or measure it yourself



Assess over the entire operating current range

0.3, 1.3 and 2.30hm resistance

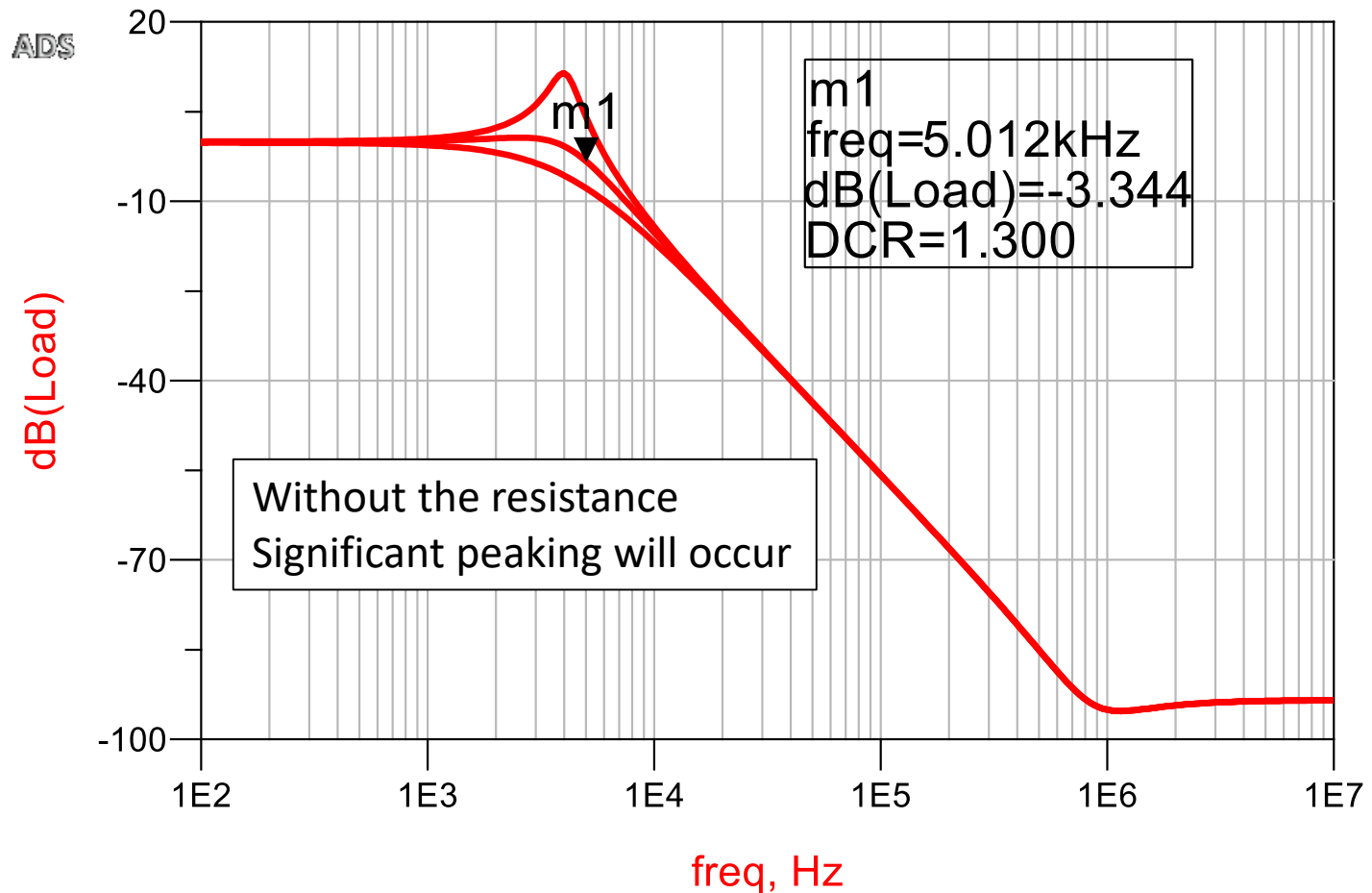

“RF” Ultra-Low-Noise Options

The precision ultra-low-noise voltage regulator offers precision in the output voltage and low noise

BUT

Count the capacitors!

Is this better or just different?

Precision voltage vs ultra-low noise

TYPICAL APPLICATION CIRCUIT


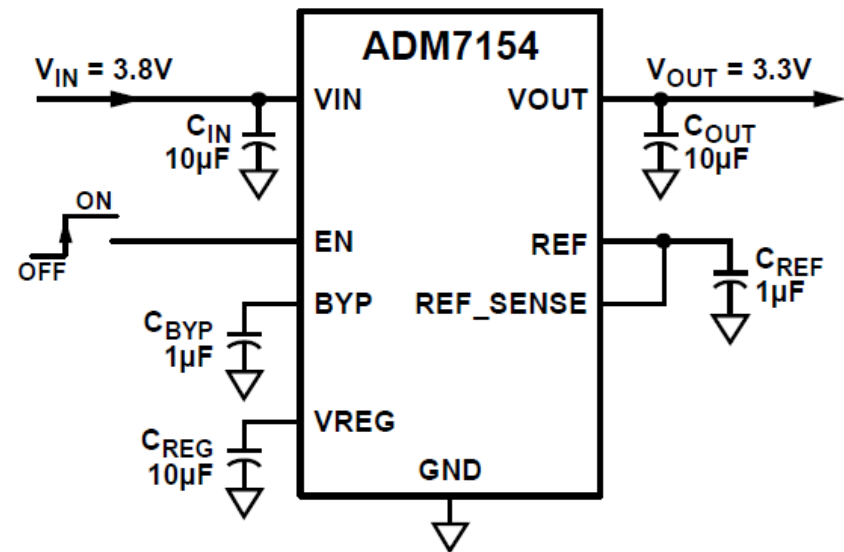


Figure 1. Regulated 3.3 V Output from 3.8 V Input


Top Tips

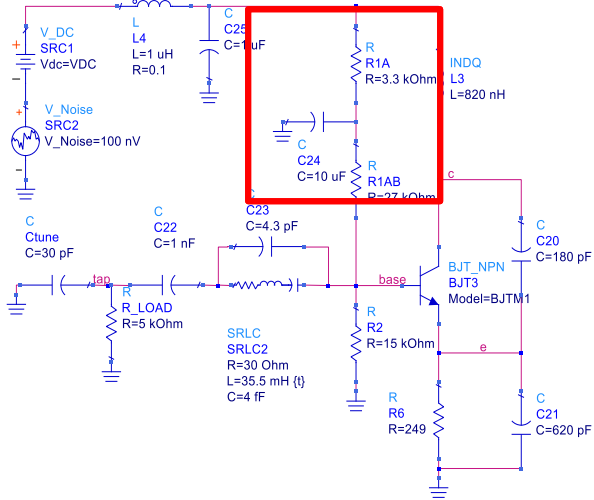


Low current bias also needs to be filtered.

Include phase noise and jitter in your simulations

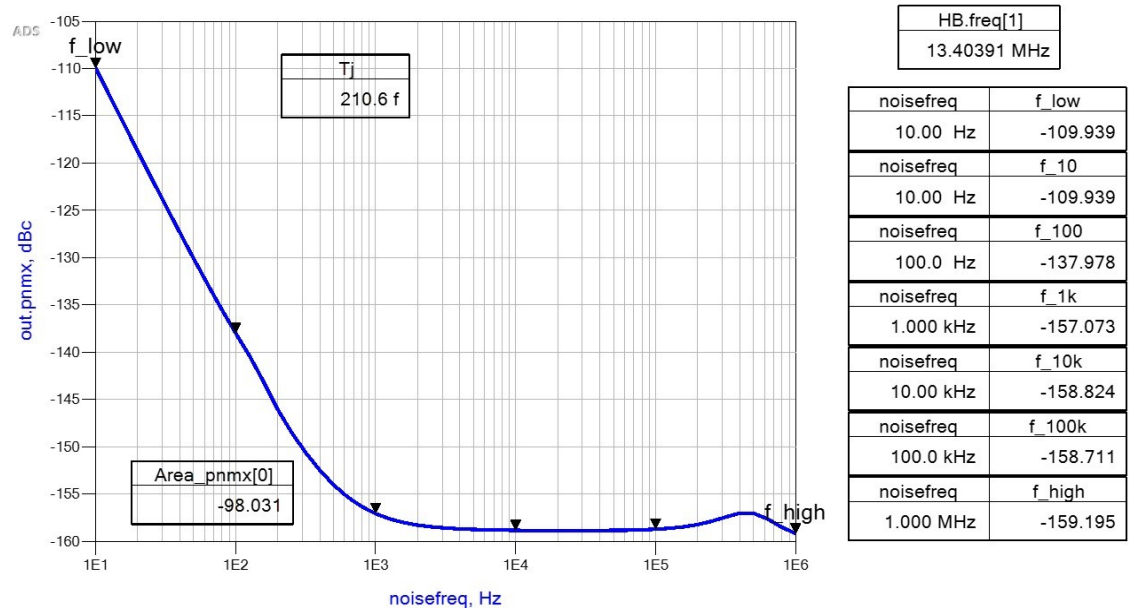
Higher value caps are generally better than lower value caps




Not all regulators are created equal

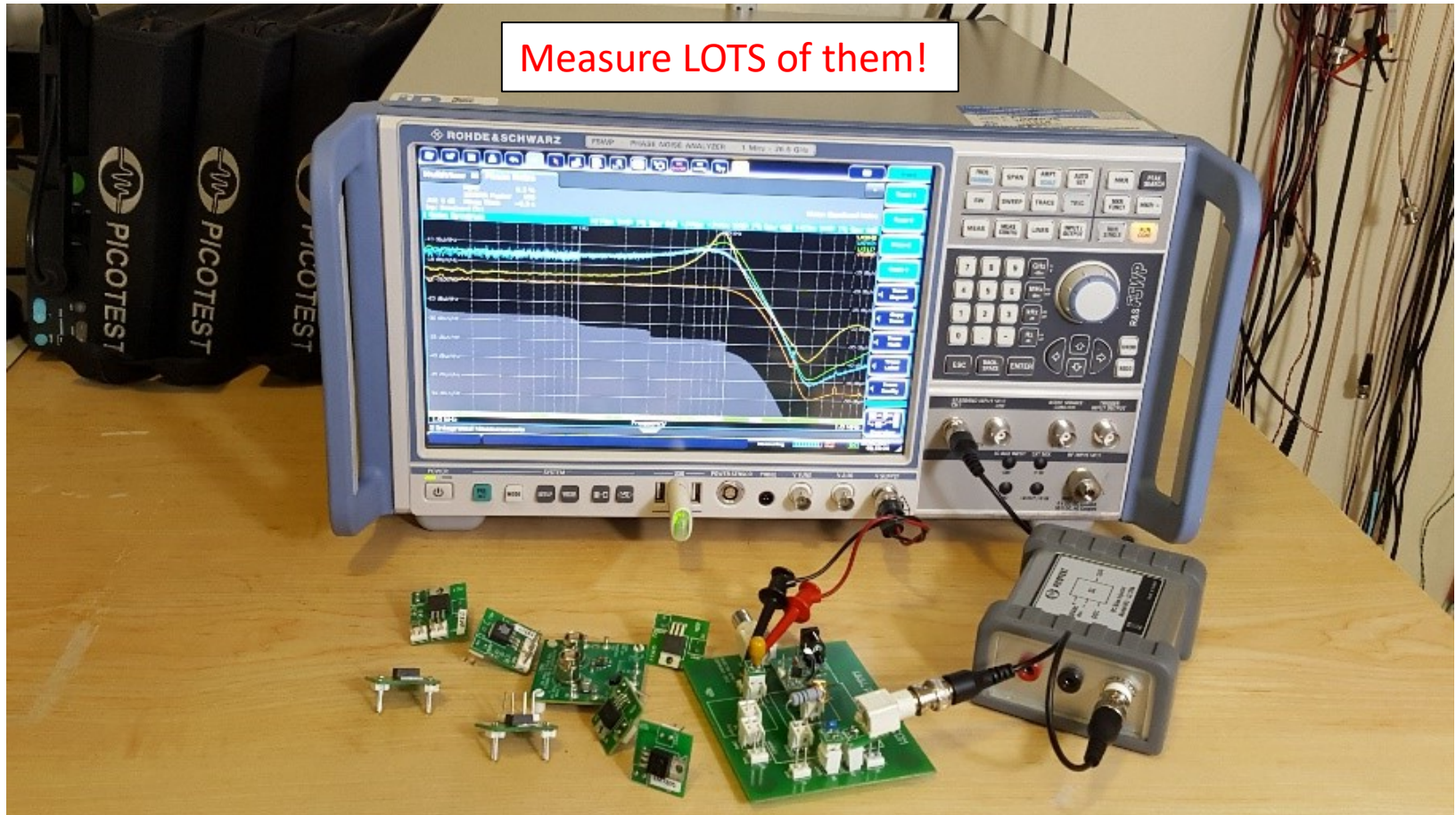

Consider all the ways noise gets in

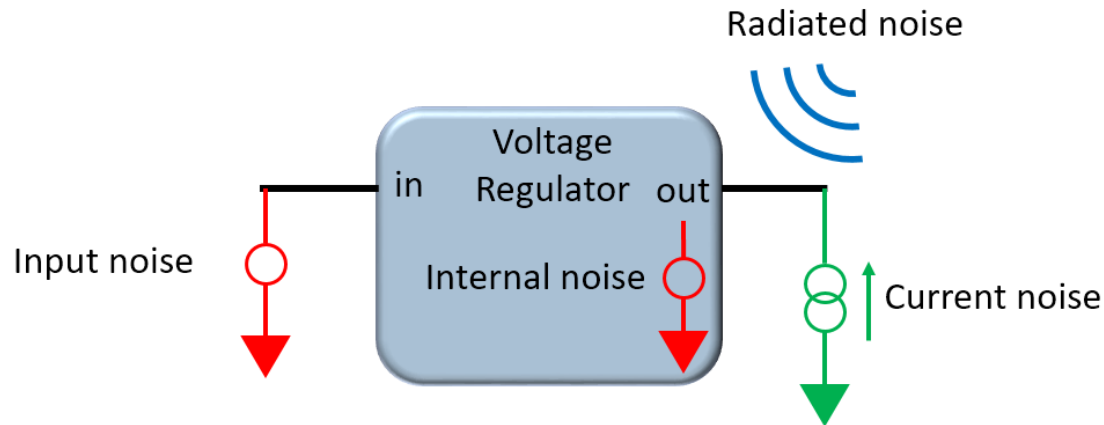

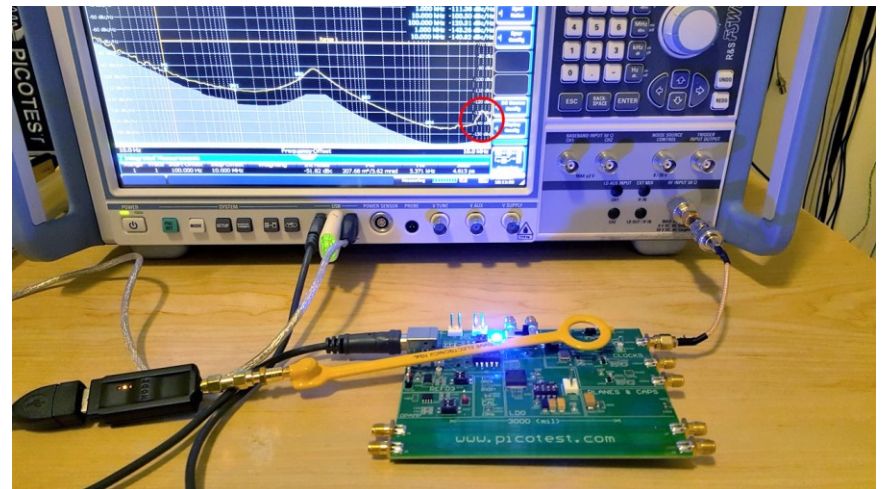Watch the coaxial cables and power interconnects also



Thanks for Attending this Session!

In this session I shared

- How to determine the circuit sensitivity to power supply noise
- How to choose the best voltage regulator
- How to design an optimum power supply noise filter
- A few of my top tips for designing power for sensitive circuits

Connect with me on LinkedIn or via email at Steve@Picotest.com

Learn more at www.picotest.com/blog

